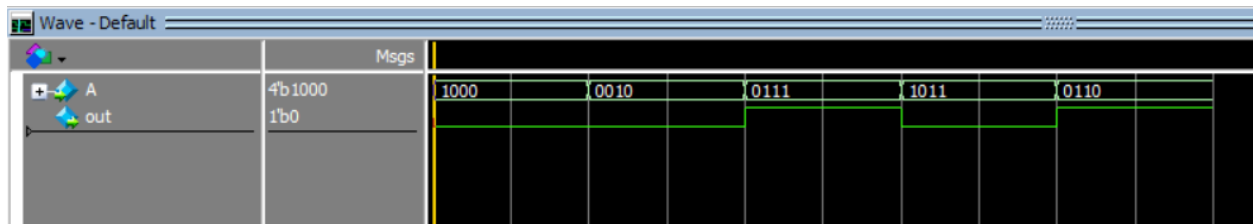


ASSAIGNMENT 1 (extra)

P1)code :

```
E: > Digital_course > design > session1 > HA > extra > p1.v > ...  
1  module problem1 (A,out);  
2  input [3:0] A ;  
3  output reg out ;  
4  
5  always @ (*) begin  
6      if (A < 8 && A > 2) begin  
7          out = 1'b1;  
8      end  
9      else out = 1'b0;  
10 end  
11 endmodule
```

Waveform snippet:



P2)


While b=0 → the output will be equal to the value of a (XOR act as a buffer)

While b=1 → the output will be equal to the value of a bar (XOR act as an inverter)

P3) code:

```
E: > Digital_course > design > session1 > HA > extra > P3.v > ...
1  module problem3 (A,B,C,F);
2  input A,B,C;
3  output F;
4  wire XOR , XNOR ;
5
6  xor (XOR,A,B);
7  xnor (XNOR,B,C);
8  and (F,XOR,XNOR,C);
9
10 endmodule
```

Waveform snippet:

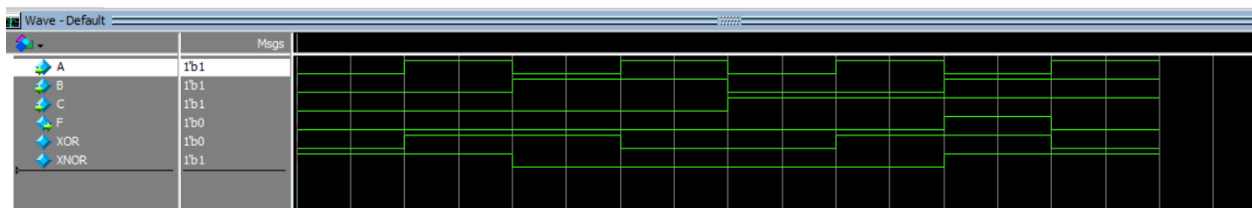

Here is the truth table


C	B	A	$A \oplus B$	$B \odot C$	F
0	0	0	0	1	0
0	0	1	1	1	1
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	0	1	0

The output will be high only when the input is (110)

P4)code :

```
E: > Digital_course > design > session1 > HA > extra > P4.v > ...  
1  module problem4 (in,s);  
2  input [2:0] in;  
3  output s;  
4  
5  assign s = ~|in ;  
6  endmodule
```


Waveform snippet:

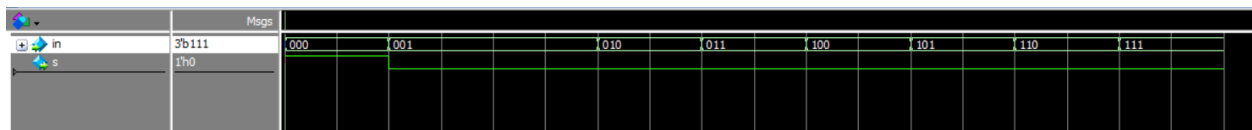

P5)code:

```
E: > Digital_course > design > session1 > HA > extra > p5.v > ...
1  module problem5 (A,B,Ainvert,Binvert,CarryIn,operation,carryout,result);
2  input A,B,Ainvert,Binvert, CarryIn ;
3  input [1:0] operation ;
4  output carryout ;
5  output reg result ;
6  wire muxA , muxB , AND , OR ;
7  wire [1:0] sum;
8  assign muxA = (Ainvert == 0) ? A: ~A ;
9  assign muxB = (Binvert == 0) ? B: ~B ;
10 and (AND,muxA,muxB);
11 or (OR,muxA,muxB);
12 assign sum = muxA + muxB +CarryIn ;
13 assign carryout = sum[1];
14
15 always @(*) begin
16     case (operation)
17         2'b00 : result = AND;
18         2'b01 : result = OR;
19         2'b10 : result = sum[0];
20         2'b11 : result = 0;
21     endcase
22 end
23 endmodule
```

Waveform snippet:

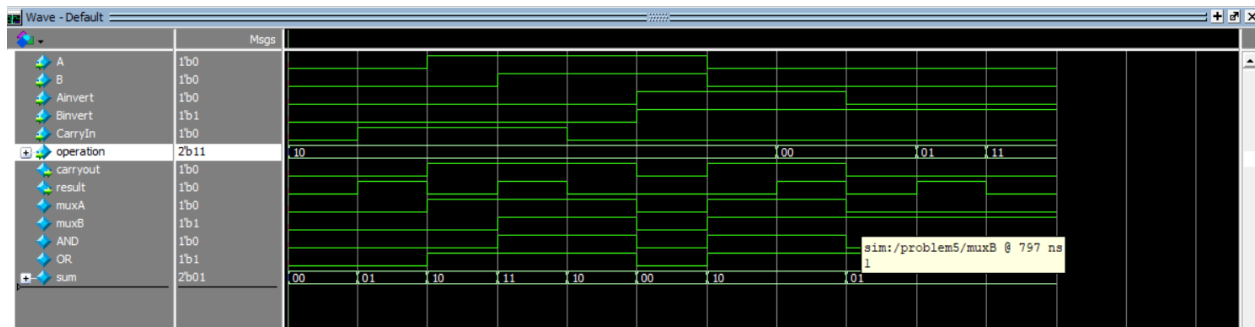

Here is the github link for all code files used in assignment